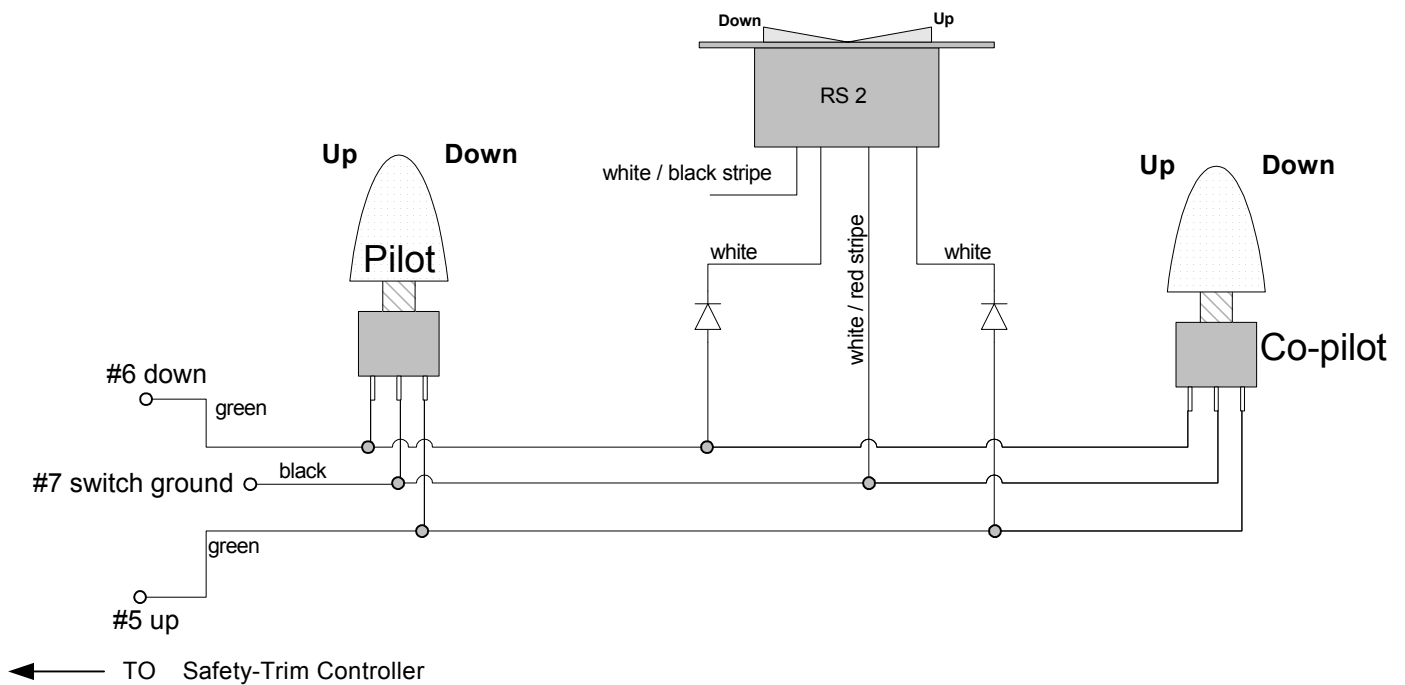


Application Note #2

Using Ray Allen RS 2 Rocker switch with additional "hat switches"



Note: Diodes may be any general purpose diode such as 1N914 or 1N4004

Note: RAY ALLEN Rocker Switch RS2 is of a custom design, in the neutral position the white wires are shorted together

Note: Aileron or Rudder trim switches may be wired in the same manner.